

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

FINAL EXAMINATION

TRIMESTER 2, 2017/2018

DET5058 – DIGITAL ELECTRONICS
(DEE)

9 March 2018
3.00pm – 5.00pm
(2 Hours)

INSTRUCTIONS TO STUDENT

1. This question paper consists of 6 pages (5 pages with 4 questions and 1 page for appendix).
2. Answer **ALL** questions. All necessary working steps must be shown.
3. Write all your answers in the answer booklet provided.

QUESTION 1 [25 Marks]

- a) Provide **FOUR** analog quantities that are normally converted into digital signals. [4 marks]
- b) Name the **FOUR** component that completes a computer system. [4 marks]
- c) One of the advantage of digital systems over analog systems is “digital systems are less affected by noise”. Explain why. [2 marks]
- d) Convert the BCD number 00110111100001100001 into:
- (i) Decimal
 - (ii) Binary
 - (iii) Octal
 - (iv) Hexadecimal
 - (v) Gray
- [10 marks]
- e) Given 10001111_2 and 11110011_2 are both in 2's complement form.
- (i) Add the numbers in 8-bit 2's complement form. [2 marks]
 - (ii) State whether overflow occurred or not. Support your statement through redoing the addition in decimal and evaluating the addition result. [3 marks]

Continued...

QUESTION 2 [40 Marks]

Given a Boolean expression $X = \overline{\overline{A}\overline{B}\overline{C}} \cdot \overline{\overline{A}\overline{B}} + \overline{\overline{B}\overline{C}} \cdot \overline{\overline{B}\overline{C}\overline{D}}$, solve the following questions.

- Draw the logic diagram of the Boolean expression. [7 marks]
- Prove that the expression can be reduced to $X = \overline{A}\overline{B} + BC + BD$ by using rules of Boolean algebra. [8 marks]
- Provide the truth table for the Boolean expression. [5 marks]
- Based on the provided truth table, provide the standard SOP expression in terms of algebraic function. [3 marks]
- Assuming don't care condition exist, where $d(A, B, C, D) = \sum m(0, 1, 2, 3)$, state whether the Boolean expression can be further reduced as compared to reduced expression in (b). You may apply Karnaugh map to prove your statement. [7 marks]
- Implement the reduced Boolean expression in (e) using NAND gates only. [4 marks]
- Draw the output waveform for the output expression based on the given input waveforms in Figure 1. Ignore don't care conditions introduced in question (e).

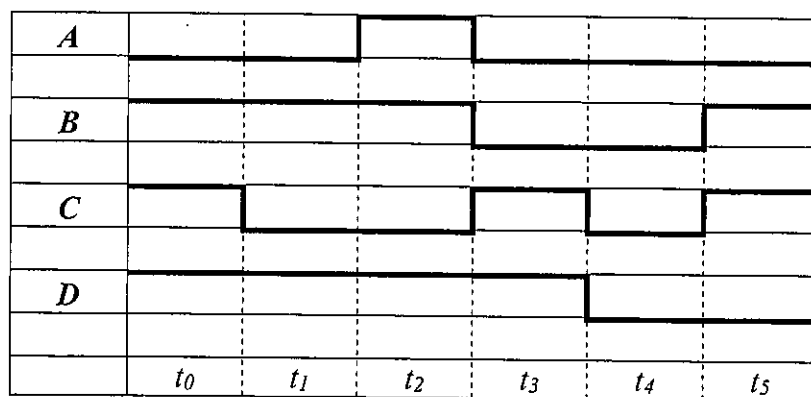


Figure 1

[6 marks]

Continued...

QUESTION 3 [20 Marks]

- a) Complete the truth table representing full subtractor below. Note that, $A - B = D$.

B_{in}	A	B	B_{out}	D
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

[8 marks]

- b) Name the combinational logic represented by the circuit diagram in Figure 2, and produce the output expression for the combinational logic.

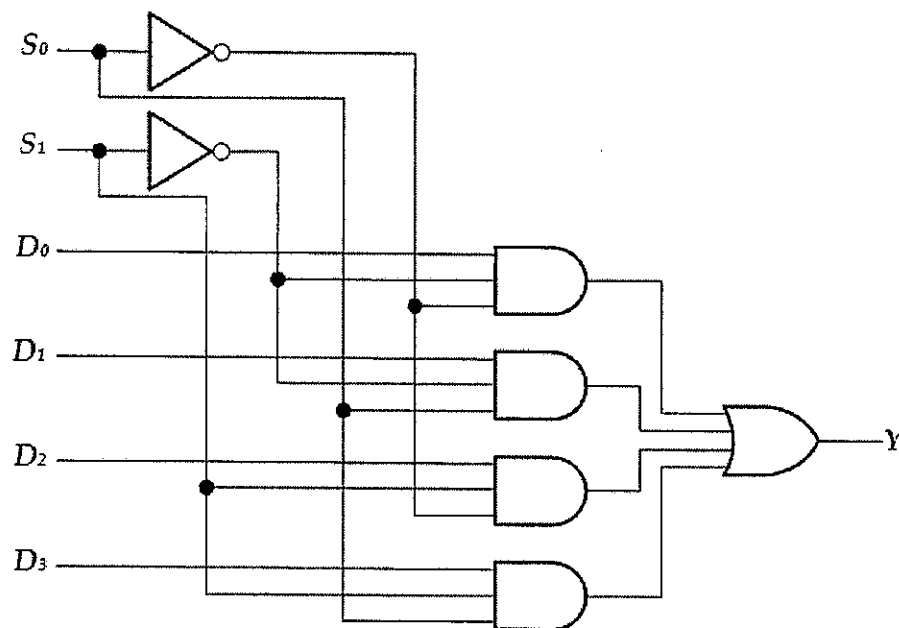


Figure 2

[5 marks]

Continued...

QUESTION 3 (Continued)

- c) Based on your answer in (b), draw the output waveform Y , based on the given input waveforms in Figure 3.

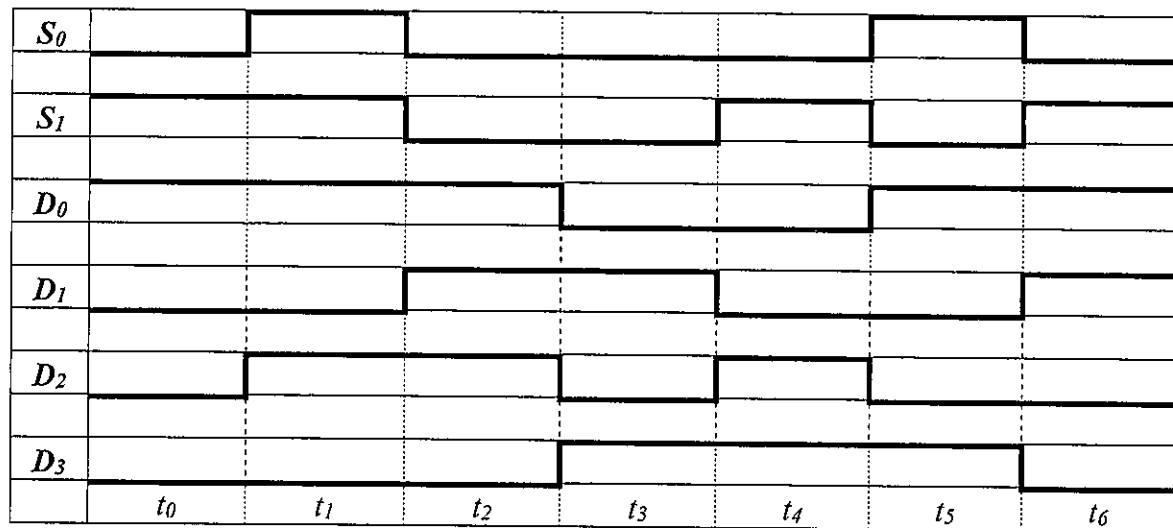


Figure 3

[7 marks]

Continued...

QUESTION 4 [15 Marks]

- a) Name the latches/flip-flops represented by the logic symbol in Figure 4.

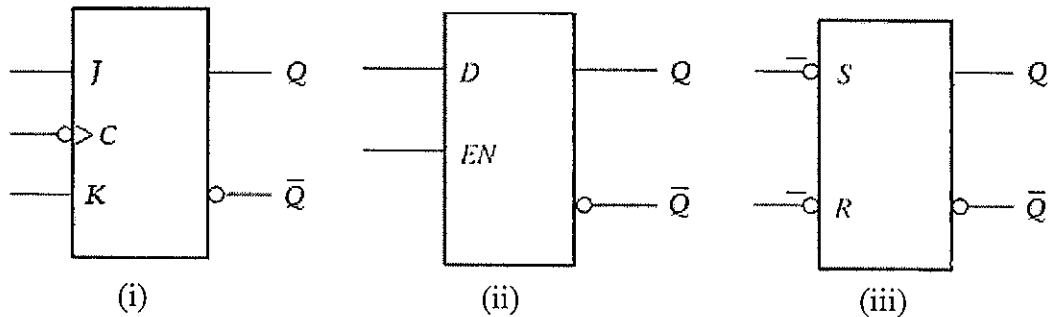


Figure 4

[6 marks]

- b) If the latches/flip-flops in Figure 4 is arranged as in Figure 5, draw the output waveforms of Q_1 , \bar{Q}_1 , Q_2 , \bar{Q}_2 and Q_3 , \bar{Q}_3 , based on the given input waveforms in Figure 6. Assume all latches/flip-flops are initially LOW.

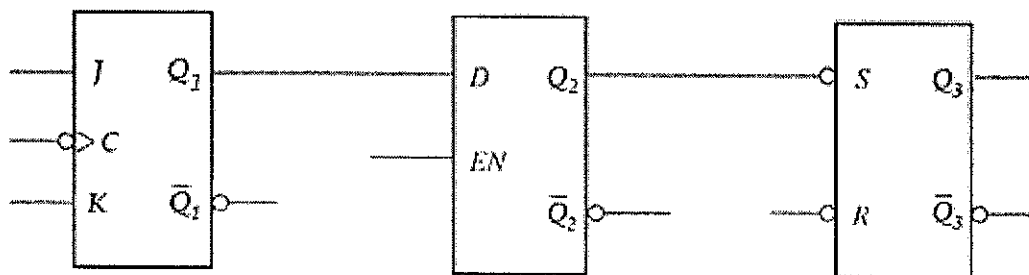


Figure 5

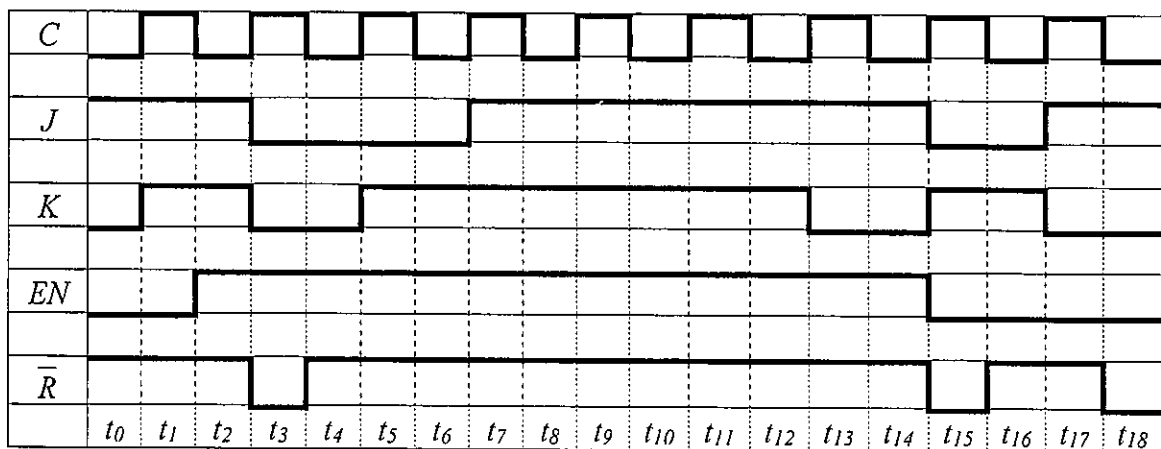


Figure 6

[9 marks]

End of Page.

APPENDIX: RULES OF BOOLEAN ALGEBRA

1. $A + 0 = A$
2. $A + 1 = 1$
3. $A \cdot 0 = 0$
4. $A \cdot 1 = A$
5. $A + A = A$
6. $A + \bar{A} = 1$
7. $A \cdot A = A$
8. $A \cdot \bar{A} = 0$
9. $\bar{\bar{A}} = A$
10. $A + AB = A$
11. $A + \bar{A}B = A + B$
12. $(A + B)(A + C) = A + BC$